

《继电保护原理》答案

第一章 电力系统继电保护的基本概念和要求

一、单选题

1	2	3	4	5	6	7	8	9	10
B	B	A	C	D	B	B	B	A	B
11	12	13	14	15	16	17	18	19	20
C	C	C	C	B	A	B	D	B	B
21	22	23	24	25	26	27	28	29	30
D	B	D	C	D	C	C	D	D	B
31	32	33	34	35	36	37	38	39	40
B	C	B	B	C	C	A	D	A	A
41	42	43	44	45	46	47	48	49	50
B	B	B	A	A	A	B	B	C	C
51	52	53	54	55					
C	C	A	B	B					

二、多选题

1	2	3	4	5	6	7	8	9	10
AD	ABC	AB	BCD	ABC	ABCD	AC	ABCD	AD	ABCD
11	12	13	14	15	16	17	18	19	20
ABCD	BCD	ABC	ABCD	ABCD	ABCD	ABCD	AC	BCD	AB
21	22	23	24	25	26	27	28	29	30
ABC	AB	ABCD	AC	AB	ABC	ACD	ACD	ACD	AC
31	32	33	34	35	36				
ABC	AD	AB	BD	ABC	BC				

三、判断题

1	2	3	4	5	6	7	8	9	10
A	B	B	A	B	A	B	B	A	A
11	12	13	14	15	16	17	18	19	20
A	A	B	B	B	A	B	A	A	B
21	22	23	24	25	26	27	28	29	30
B	B	A	A	B	A	B	B	B	A
31	32	33	34	35	36	37	38	39	40
A	A	B	B	A	A	B	B	A	B
41	42	43	44	45	46	47	48	49	50
B	A	B	A	B	A	A	B	B	A

第二章 阶段式电流保护配合原理、构成和整定计算

一、单选题

1	2	3	4	5	6	7	8	9	10
A	B	B	C	D	C	A	C	B	C
11	12	13	14	15	16	17	18	19	20
B	C	D	A	B	B	A	B	D	C
21	22	23	24	25	26	27	28	29	30
A	C	C	B	A	B	C	D	B	C
31	32	33	34	35	36	37	38	39	40
A	A	A	B	A	B	B	D	A	A
41	42	43	44	45	46	47	48	49	50
C	D	A	B	B	A	B	B	B	D
51	52	53	54	55	56	57	58	59	60
A	B	A	B	A	A	D	C	B	B
61	62	63	64	65	66	67	68	69	70
D	D	D	C	C	D	C	B	C	D
71	72	73	74	75	76	77	78	79	80
D	A	B	B	A	B	A	C	D	B

81	82	83	84	85					
D	A	C	D	D					

二、多选题

1	2	3	4	5	6	7	8	9	10
AB	AB	BCD	AB	AB	AB	AB	ABCD	AB	ABC
11	12	13	14	15	16	17	18	19	20
AB	AB	ACD	BC	ABC	BC	AB	AB	AB	AB
21	22	23	24	25	26	27	28	29	30
ABC	CD	AC	ABC	ABC	AB	ABD	AD	ABCD	BC
31	32								
AB	BC								

三、判断题

1	2	3	4	5	6	7	8	9	10
A	A	A	A	B	B	B	A	A	A
11	12	13	14	15	16	17	18	19	20
B	B	A	B	A	A	B	B	A	B
21	22	23	24	25	26	27	28	29	30
B	A	A	A	A	B	B	B	B	A
31	32	33	34	35	36	37	38	39	40
B	B	A	A	A	A	A	A	A	A
41	42	43	44	45	46	47	48		
A	A	B	B	B	B	B	A		

第三章 距离保护的工作原理、动作特性和整定计算

一、单选题

1	2	3	4	5	6	7	8	9	10
C	B	B	B	B	C	B	D	B	C
11	12	13	14	15	16	17	18	19	20
B	C	B	A	B	B	C	D	D	C
21	22	23	24	25	26	27	28	29	30
B	B	B	C	A	C	D	B	B	A
31	32	33	34	35	36	37	38	39	40
C	A	A	A	A	A	C	B	C	A
41	42	43	44	45	46	47	48	49	50
D	D	D	C	B	B	A	A	A	B
51	52	53	54	55	56	57	58	59	60
D	B	A	A	C	B	A	C	A	A
61	62	63	64	65	66	67	68	69	70
A	B	B	B	B	A	A	A	B	D
71	72	73	74	75	76	77	78	79	80
A	B	C	C	B	C	C	A	B	B
81	82	83	84	85	86	87	88	89	90
B	B	A	B	D	C	B	C	C	B
91	92								
C	B								

二、多选题

1	2	3	4	5	6	7	8	9	10
AB	ABC	AB	ABC	ABC	ACD	AD	ABCD	ABCD	AB
11	12	13	14	15	16	17	18	19	20

ABCD	AB	ABCD	ABCD	AB	ABCD	BD	ABCD	AB	AC
21	22	23	24	25	26	27	28		
CD	ACD	ABCD	CD	ABD	CD	ABCD	BCD		

三、判断题

1	2	3	4	5	6	7	8	9	10
A	B	A	B	B	A	A	B	B	B
11	12	13	14	15	16	17	18	19	20
B	B	A	A	A	A	B	A	B	A
21	22	23	24	25	26	27	28	29	30
A	A	A	A	A	B	B	A	A	B
31	32	33	34	35	36	37	38	39	40
A	A	A	A	A	A	A	A	A	A
41	42	43	44	45	46	47	48	49	50
B	A	A	A	B	A	A	B	A	A
51	52	53	54	55	56	57	58	59	60
A	A	A	B	A	A	A	B	A	B
61									
A									

第四章 输电线路纵联保护原理

一、单选题

1	2	3	4	5	6	7	8	9	10
A	C	A	B	C	C	D	A	D	B
11	12	13	14	15	16	17	18	19	20
A	B	A	B	B	B	C	A	C	C
21	22	23	24	25	26	27	28	29	30
B	B	D	C	B	B	B	A	C	C
31	32	33	34	35	36	37	38	39	40
B	A	D	B	B	B	A	A	A	A

41	42	43	44	45	46	47	48	49	50
B	A	A	C	C	A	B	A	A	C
51	52	53	54	55	56	57	58	59	60
C	C	A	D	D	D	C	A	B	C
61	62	63	64	65	66	67	68	69	70
A	A	A	A	A	B	B	D	A	B
71	72	73	74						
B	A	B	A						

二、多选题

1	2	3	4	5	6	7	8	9	10
ABD	ABCD	ACD	ABC	AB	ABC	AB	ABCD	AB	ABC
11	12	13	14	15	16	17	18	19	20
BC	ABC	ABCD	ABC	AB	ABC	AB	ABCD	ABC	AB
21	22	23	24	25	26	27	28	29	30
ABC	ABCD	AB	ACD	AC	ABC	ABCD	AC	AD	ABCD
31									
BC									

三、判断题

1	2	3	4	5	6	7	8	9	10
A	B	A	A	A	A	B	A	A	B
11	12	13	14	15	16	17	18	19	20
A	A	B	A	A	A	B	B	A	B
21	22	23	24	25	26	27	28	29	30
A	A	A	A	A	B	B	A	B	A
31	32	33	34	35	36	37	38	39	40
B	A	A	B	B	B	A	B	A	A
41	42	43	44	45	46	47	48	49	50
A	A	A	A	A	A	A	A	A	A
51	52	53	54	55	56	57	58	59	60
A	A	A	A	B	A	A	B	A	A

61									
B									

第五章 输电线路自动重合闸的作用和要求

一、单选题

1	2	3	4	5	6	7	8	9	10
A	A	D	A	C	B	D	A	A	B
11	12	13	14	15	16	17	18	19	20
A	A	A	A	C	A	A	A	A	D
21	22	23	24	25	26	27	28	29	30
A	A	A	B	B	B	B	A	C	B
31	32	33	34	35	36	37	38	39	40
C	C	A	C	C	D	A	B	C	B
41	42	43	44	45	46	47	48	49	
A	A	A	A	A	A	B	C	A	

二、多选题

1	2	3	4	5	6	7	8	9	10
ABC	ABC	AD	AB	ABC	ABC	CD	ABC	BCD	ABCD
11	12	13	14	15	16	17	18	19	20
ABC	ABC	ABC	AB	ABC	ABCD	AD	ABC	AB	ABC
21	22	23	24	25	26	27			
ABC	ABC	AB	ABCD	ABC	ABC	ABCD			

三、判断题

1	2	3	4	5	6	7	8	9	10
A	A	A	A	A	A	B	B	A	A
11	12	13	14	15	16	17	18	19	20
B	A	B	B	B	A	A	A	A	A
21	22	23	24	25	26	27	28	29	30

A	A	B	B	A	A	B	A	A	A
31	32	33							
B	B	B							

第六章 变压器、母线的主要故障类型、保护配置和特殊问题

一、单选题

1	2	3	4	5	6	7	8	9	10
C	A	B	C	B	B	A	B	B	D
11	12	13	14	15	16	17	18	19	20
A	D	A	C	D	D	D	B	A	A
21	22	23	24	25	26	27	28	29	30
A	C	C	C	B	C	B	B	B	B
31	32	33	34	35	36	37	38	39	40
B	A	B	D	C	B	B	A	A	D
41	42	43	44	45	46	47	48	49	50
A	C	A	B	B	C	C	B	C	B
51	52	53	54	55	56	57	58	59	60
B	A	A	C	A	D	A	B	D	C
61	62	63	64	65	66	67	68	69	70
C	D	C	B	C	C	C	C	A	B
71	72	73	74	75	76	77	78	79	80
B	A	D	B	D	A	A	B	A	A
81	82	83	84	85	86	87	88	89	90
C	A	C	C	A	B	B	B	B	D
91	92	93	94	95	96	97	98	99	100
C	B	D	A	A	B	B	A	A	A
101	102	103	104	105	106	107	108	109	110
C	B	D	A	A	A	A	A	A	A

111	112	113	114	115	116	117	118	119	120
C	B	D	A	D	C	A	B	B	A
121	122	123	124	125	126	127	128	129	130
D	B	B	B	B	C	C	C	A	B
131									
D									

二、多选题

1	2	3	4	5	6	7	8	9	10
ABCD	ABCD	ABCD	ACD	ABCD	ABCD	ABC	ABCD	ABCD	ABCD
11	12	13	14	15	16	17	18	19	20
ABC	ABC	ABCD	ABC	ABCD	AD	ABCD	ABCD	ACD	BC
21	22	23	24	25	26	27	28	29	30
AB	ABD	ABCD	AB	ABCD	ABCD	AB	ABC	AB	AD
31	32	33	34	35	36	37	38	39	40
ABC	AB	ABCD	ABC	ABC	ABC	AB	AB	ABC	ABCD
41	42	43	44	45	46	47	48	49	50
BCD	ABC	ABD	AB	AB	ABC	ABCD	AB	ABC	AC

三、判断题

1	2	3	4	5	6	7	8	9	10
B	A	A	B	B	A	B	B	A	B
11	12	13	14	15	16	17	18	19	20
A	A	A	B	A	A	A	A	B	A
21	22	23	24	25	26	27	28	29	30
A	B	A	B	B	B	A	A	A	A
31	32	33	34	35	36	37	38	39	40
B	B	B	A	A	A	B	A	B	B
41	42	43	44	45	46	47	48	49	50
A	A	B	B	A	B	B	B	B	A
51	52	53	54	55	56	57	58	59	60
A	A	A	A	A	A	A	A	A	A

61	62	63	64	65	66	67	68	69	70
A	A	A	B	A	A	B	A	B	B
71	72	73	74	75	76	77	78	79	80
B	B	B	B	A	A	B	A	A	A
81	82	83	84	85	86	87	88	89	90
A	A	A	A	B	A	A	A	B	A
91	92	93	94	95	96				
A	A	A	B	B	B				

第七章 互感器、控制回路

一、单选题

1	2	3	4	5	6	7	8	9	10
B	A	B	B	A	A	A	C	A	B
11									
B									

二、多选题

1	2	3	4	5	6	7	8	9	10
ABD	AC	ABCD	ABCD	AC	ABCD	ABD	ABD	AC	AD

三、判断题

1	2	3	4	5	6	7	8	9	10
B	B	A	B	B	B	A	B	A	A
11	12	13	14	15	16	17	18	19	20
A	B	B	B	A	A	B	A	A	A
21	22								
A	A								

第八章 微机保护

一、单选题

1	2	3	4	5	6	7	8	9	10
A	B	D	D	A	A	B	B	C	C
11	12	13	14	15	16	17	18	19	
A	B	B	B	C	A	A	D	A	

二、多选题

1	2	3	4	5					
ABCD	ABC	ABCD	AD	ABCD					

三、判断题

1	2	3	4	5	6	7	8	9	10
A	A	A	A	B	A	B	B	A	A
11	12	13	14						
B	A	A	A						

衡真教育